

3] a)
$$V_{in}(k) = V_R + V_c + V_L$$

 $V_{in}(k) = RC \frac{dV_{out}}{dk} + CL \frac{d^2V_{out}}{dt^2} + V_{out}$
b) $V_{in}(w) = RC \int w V_{in}(w) + CL \frac{d^2V_{out}}{dt^2} + V_{out}$

$$V_{ih}(\omega) = V_{out}(\omega) \left[j\omega RC - \omega^{2}CL + 1 \right]$$

$$\frac{V_{out}(\omega)}{V_{ih}(\omega)} = \frac{1}{j\omega RC - \omega^{2}CL + 1} = H(\omega)$$

$$\sqrt{1-2w^{2}CL+w^{4}c^{2}L^{2}+w^{2}R^{2}c^{2}}$$

$$H(w) = \left(1 - 2w^{2}CL + w^{4}c^{2}L^{2} + w^{2}R^{2}c^{2}\right)^{\frac{1}{2}}$$

$$H(w) = \left(1 - 2w^{2}CL + w^{4}c^{2}L^{2} + w^{2}R^{2}C^{2}\right)^{-\frac{1}{2}}$$

$$\frac{dH(w)}{dw} = \left(\frac{1}{1 - 2w^{2}CL + w^{4}c^{2}L^{2} + w^{2}R^{2}C^{2}}\right) \cdot \left(\frac{1}{1 - 2w^{2}CL + w^{4}C^{2}L^{2} + w^{4}C^{2}L^{2}}\right) \cdot \left(\frac{1}{1 - 2w^{2}CL + w^$$

$$\sqrt{\frac{2CL-R^{2}C^{2}}{2C^{2}L^{2}}}=w^{-1}+U^{-1}$$

$$\frac{1}{+ w^{4}c^{2}L^{2} + w^{2}R^{2}c^{2}}$$

$$O = -4CL + 4g^{2}L^{2}w^{2} + 2R^{2}c^{2}$$

$$O = -2CL + 2t^{2}L^{2}w^{2} + 2t^{2}c^{2}$$

$$\sqrt{\frac{1}{CL} - \frac{R^2}{7L^2}} = \omega$$



